

The Paradox of Power Loss in a Lossless Infinite Transmission Line

Ashok K. Singal

Astronomy and Astrophysics Division, Physical Research Laboratory, Navrangpura,
Ahmedabad - 380 009, India

E-mail: asingal@prl.res.in

October 2015

Abstract. We discuss here the famous paradox of a continuous power drainage from the source at the input of an otherwise lossless infinite transmission line. The solution of the paradox lies in the realization that in an open-circuit finite transmission line/ladder network, there is an incident as well as a reflected wave and the input impedance is determined by the superposition of both waves. It is explicitly shown that the reactive input impedance of even a single block, comprising say a simple LC circuit, is determined at all driving frequencies from the superposition of incident and reflected waves, and that the input impedance remains reactive in nature (i.e., an imaginary value) even when additional blocks are added indefinitely. However in a ladder network or transmission line, taken to be *infinite right from the beginning*, there is no reflected wave (assuming the circuit to be ideal with no discontinuities en route). Thus the source while continuously supplying power in the forward direction, does not retrieve it from a reflected wave and unlike in the case of a finite line, there is a net power loss. This apparently lost energy ultimately appears in the electromagnetic fields in the reactive elements (capacitances and inductances which to begin with had no such stored energy), further down the line as the incident wave advances forward. It is also shown that radiation plays absolutely no role in resolving this intriguing paradox.

PACS numbers: 01.50.-i, 07.50.-e, 78.20.Ci, 84.30.-r, 84.40.Az

1. Introduction

A transmission line is a channel for transmitting electric signals or power from one point to another along a guided path [1, 2, 3, 4]. A line could be of a finite length or be of infinite length (at least in principle). A circuit comprising lumped parameters is generally called a ladder network, on the other hand if it consists of a continuous distribution of parameters, then it is usually called a transmission line. The two are almost identical in their behavior [1]. The elements of a transmission line could be either reactances (with no power dissipation within them) like capacitances or inductances, or could comprise resistances or shunt leakage conductances, which dissipate power into heat. Most lines will have a mixture of reactances and dissipative elements. An ideal

transmission line may be thought of as the one which delivers signal or power across its length without any dissipation on the way. Intuitively one would think a line devoid of elements like resistances should behave as a lossless line without a continuous power drainage from the source at the input, and this does seem to hold true for a line of finite length. However, for an infinite line, even if there were no resistive elements along its length that could dissipate power, the line presents a *real value* of input impedance, implying that power will be drained from the source at a constant rate [5].

Where does this energy go as it is not dissipated in the inductors and capacitors of the circuit? For this Feynman [4] writes “But how can the circuit continuously absorb energy, as a resistance does, if it is made only of inductances and capacitances? *Answer:* Because there are an infinite number of inductances and capacitances, so that when a source is connected to the circuit, it supplies energy to the first inductance and capacitance, then to the second, to the third, and so on. In a circuit of this kind, energy is continually absorbed from the generator at a constant rate and flows constantly out into the network, supplying energy which is stored in the inductances and capacitances down the line.”

In an alternative approach [6, 7] it has been shown that the input impedance of an open-circuit ladder network, initially consisting of a finite number of blocks comprising inductors and capacitors, does not converge to a unique fixed value when additional identical blocks are added, and always yields pure imaginary (reactive) input impedance value irrespective of the number of the blocks added. The input impedance does not have a real (dissipative) part for any driving frequency, even when the number of blocks is increased indefinitely. This contradicts Feynman’s observation [4] that the infinite ladder network has an input impedance which has a real part at frequencies below certain value. It was argued afterwards [8] that a non-zero real part of impedance appears only if there is a termination in an impedance that has a real part and that a circuit consisting solely of components with purely imaginary impedances has a purely imaginary input impedance. Later the behavior of infinite ladder network, its convergence and solutions have been analyzed in a greater detail [9, 10].

In this paper we examine this intriguing paradox from a fresh view point trying to understand why two alternate approaches lead to conflicting results. We will first review the relevant characteristics of a transmission line/ladder network; the detailed description of various terms and the derivation of the formulas used can be found in standard text-books [1, 2, 3, 4]. Then we shall show how one arrives at a paradoxical result of an uninterrupted power drain in an otherwise lossless infinite transmission line. This will be followed by a brief account of the alternative approach of extending a finite ladder network by the addition of further blocks, with the circuit always comprising only reactive elements. Subsequently we shall present the resolution of the paradoxical results both for a ladder network as well as the transmission line; the resolution basically ensues the realization that there is an absence of a reflected wave in an infinite ladder network or a transmission line. Reflection plays a role in resolving the paradox was briefly mentioned in [10] but without much further elaboration, which we do here in

detail by explicitly calculating the input impedance of a finite ladder network by a superposition of incident and reflected waves. We shall demonstrate that unlike in a finite case, where a termination in a load matched to the characteristic impedance of the line could dissipate all power, or at an open-ended termination could reflect it all back towards the source, in the case of an infinite line there is no termination point to start a reflected wave (assuming of course no discontinuities along the line to trigger any reflection) and that results in the current being in phase with the voltage and power being drawn from the source.

2. A non-ideal behavior of an ideal circuit

2.1. A transmission line

A transmission line is described by its line parameters R, L, C, G , where R is the series resistance per unit length of line (including both wires), L is the series inductance per unit length of line, C is the capacitance between the two conducting wires per unit length of line and G is the shunt leakage conductance between the two conducting wires per unit length of line. For an incremental length Δz of the line, the equivalent circuit is shown in Fig. 1. The increments in voltage and current along the line are [1, 2, 3, 5],

$$\Delta V(z) = -I(z)(R + j\omega L)\Delta z \quad (1)$$

$$\Delta I(z) = -V(z)(G + j\omega C)\Delta z. \quad (2)$$

These could be written in limit $\Delta z \rightarrow 0$ as,

$$dV(z)/dz = -I(z)(R + j\omega L) \quad (3)$$

$$dI(z)/dz = -V(z)(G + j\omega C). \quad (4)$$

From Eqs. (3) and (4) one gets a general solution for voltage along the line,

$$V(z) = V_0' e^{-\gamma z} + V_0'' e^{\gamma z} \quad (5)$$

$$\gamma = \sqrt{(R + j\omega L)(G + j\omega C)} = \alpha + j\beta, \quad (6)$$

where γ is the propagation constant. The phasor part is written with an assumed $e^{j\omega t}$ time dependence throughout. Now of the two terms in Eq. (5), the first one represents a wave traveling along increasing z commencing at $z = 0$, while the second represents a wave traveling towards decreasing z which in case of an infinite line would have to start from $z = \infty$ an infinite time back and thus must be dropped. Therefore the voltage along an infinite transmission line can be written as,

$$V(z) = V_0 e^{-\gamma z} = V_0 e^{-\alpha z} e^{-j\beta z}. \quad (7)$$

From this one gets for the electric current,

$$I(z) = (V_0/Z_0) e^{-\gamma z} = (V_0/Z_0) e^{-\alpha z} e^{-j\beta z}. \quad (8)$$

Here Z_0 , the characteristic impedance of the line given by,

$$Z_0 = \sqrt{(R + j\omega L) / (G + j\omega C)}. \quad (9)$$

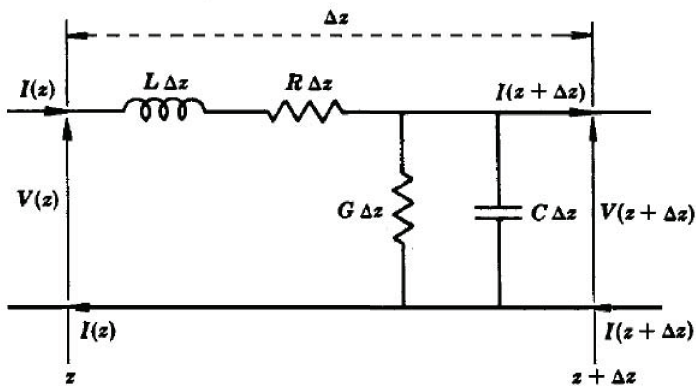


Figure 1. Increments of voltage and current over an incremental length Δz of the transmission line.

Equations (7) and (8) represent an attenuated sinusoidal wave along z , with α as the attenuation constant and $\beta = 2\pi/\lambda$ as the wave number.

For an infinite line, the input impedance (at $z = 0$) is calculated from Eqs. (7) and (8) as,

$$Z_i = V(0)/I(0) = Z_0. \quad (10)$$

In a lossless line, $R = 0$ and $G = 0$, and from Eqs. (6) we have, $\alpha = 0$ and $\beta = \omega\sqrt{LC}$, i.e., a sinusoidal wave without any attenuation along the line. But we also have $Z_i = Z_0 = \sqrt{L/C}$, i.e., its impedance has a *real* value. This is a paradox because though the transmission line contains no resistive element so there could be no Ohmic losses in the line, yet its input impedance is a pure resistance. That means for an input voltage V_0 , power will be drained from the source at the rate of $V_0^2/(2\sqrt{L/C})$ [5]. The questions therefore arise as to why does a pure resistance show up in a circuit comprising only reactances, thereby implying a continuous power drainage and where does this energy ultimately go?

The paradox can be also seen from the Smith chart where the input impedance of a lossless open-circuit line, goes through cycles when its length is varied. Not only does the input impedance not converge to a single unique value when the length of the line is increased indefinitely but also in general it is an *imaginary* value, i.e., a pure reactance [1, 2, 3] for any length of the line, which contradicts the conclusion that the infinite line presents a *real* input impedance.

2.2. A ladder network

A transmission line with distributed parameters is almost identical in behavior to a ladder network comprising lumped parameters [1], and the above paradox appears in the infinite ladder network too. A Ladder network of n blocks, with each block a symmetrical T section consisting of two $L/2$ inductances and a capacitance C , has a characteristic impedance $Z_0 = \sqrt{L/C - \omega^2 L^2/4}$ [1, 2, 3]. The number n of blocks

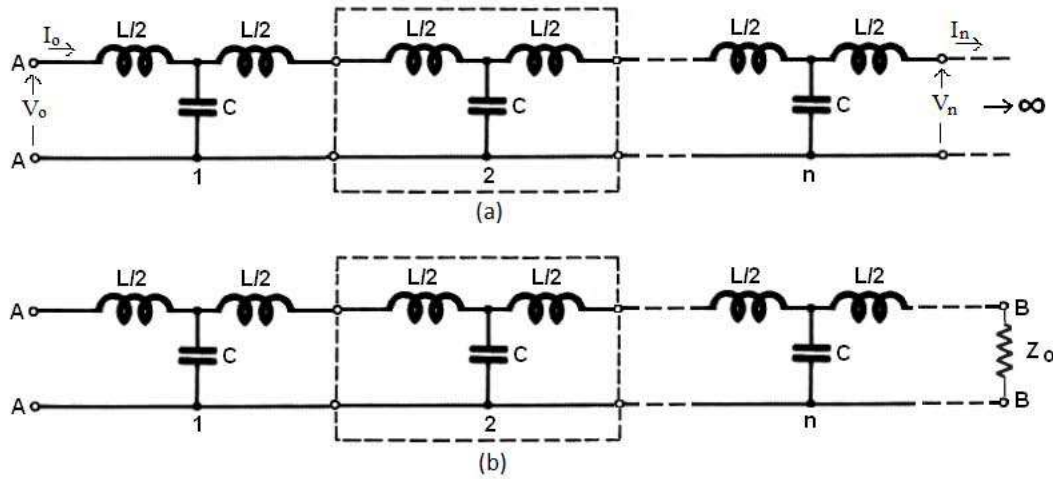


Figure 2. (a) An infinite ladder network comprising lumped parameters. (b) A finite ladder network terminated in its characteristic impedance Z_0 . A typical block in the network is shown by a rectangular box of dashed lines.

could be finite, or it could even be infinite ($n \rightarrow \infty$). Figure 2(a) shows an infinite ladder network while Fig. 2(b) shows a finite ladder network, but terminated in its characteristic impedance $Z_0 = \sqrt{L/C - \omega^2 L^2/4}$.

A solution for the input impedance Z_i of the infinite network is obtained in the following manner [4, 6, 7, 11, 12]. Since adding another block to the beginning of an infinite ladder network does not change the input impedance (it still remains the same infinite network), Z_i must equal the impedance of a circuit having a single block terminated in a load impedance equal to Z_i . Therefore we have,

$$Z_i = \frac{j\omega L}{2} + \frac{(Z_i + j\omega L/2)(1/j\omega C)}{Z_i + j\omega L/2 + 1/j\omega C}, \quad (11)$$

which has a solution,

$$Z_i = \sqrt{L/C - \omega^2 L^2/4}. \quad (12)$$

The input impedance of the infinite network equals its characteristic impedance, i.e., $Z_i = Z_0$, and the circuit behaves as if it were terminated in Z_0 somewhere along the line as in Fig. 2(b). Now for $\omega < \omega_0 = 2/\sqrt{LC}$, Z_i is a *real* value. This leads to the same paradox as for the infinite transmission line of distributed parameters – how come a circuit containing only purely imaginary impedances has for its input impedance a *real* value which could absorb energy continuously?

3. Where does the energy disappear? – Could radiation losses be the answer?

Could the energy be lost into the surrounding medium by the process of radiation, with $Z_0 = \sqrt{L/C}$ as the radiation resistance? In transmission line or ladder network

containing resistive elements, power loss by the source is fully accounted for by the energy dissipation in the circuit, for any value of R and G .

Consider the lossy infinite line (i.e., with R and G non-zero), where input power from the source is [5],

$$P_i = [V_0^2/(2|Z_0|)] \cos(\angle Z_0) = [V_0^2/(2|Z_0|^2)] Re(Z_0). \quad (13)$$

On the other hand the power dissipated in an infinitesimal line element (Fig. 1) is,

$$dP_d = (1/2) (|I(z)|^2 R + |V(z)|^2 G) dz \quad (14)$$

$$= (V_0^2/2) \left[\left(R/|Z_0|^2 \right) + G \right] e^{-2\alpha z} dz \quad (15)$$

Hence the total power dissipated in the infinite line is

$$P_d = (V_0^2/2) \left[\left(R/|Z_0|^2 \right) + G \right] \int_0^\infty e^{-2\alpha z} dz \quad (16)$$

$$= (V_0^2/2) \left[\left(R/|Z_0|^2 \right) + G \right] / (2\alpha) \quad (17)$$

Substitution for $|Z_0|$ and α shows that $P_d = P_i$ [5], and all power losses are accounted for without anything going into radiation. This is true for all R and G , in particular even when in limit $R \rightarrow 0$ and $G \rightarrow 0$. Now it cannot happen that when $R = 0$ and $G = 0$ radiation suddenly shows up into picture from somewhere. Further, even in a lossless line, all the power (assumed to be lost by the source) can at any stage be either reflected back by making the circuit open just after that point, or it could be consumed by terminating the line in its characteristic impedance, irrespective of the length of the line up to that stage. This implies that up to any *arbitrarily selected length* of the line, the radiation losses had not yet taken place. Therefore for resolving this paradox there does not seem any scope for radiation hypothesis at all and a satisfactory resolution of the paradox lies elsewhere.

4. The paradox reappears!

Actually while writing Eq. (11) for Z_i one implicitly assumed that the infinite series *converges* to a unique value and it is only under this existence supposition that a unique solution Eq. (12) could be obtained. If the series does not converge, then of course this basic assumption itself breaks down and the solution obtained thereby may not represent a true value.

On the other hand if one started with an open-circuit ladder network of a finite number of identical blocks comprising inductors and capacitors, and then added more similar blocks, the input impedance does not converge to a unique fixed value even when the number of blocks is increased indefinitely. Moreover, the input impedance always turns out to be a pure imaginary value with no real (dissipative) part for any driving frequency, even when the number of blocks approaches infinity.

It seems that the infinite ladder networks of type in Fig 2(a) may have different answers for the input impedance, and thereby implying different power consumptions depending upon the method of solution. Hence a paradox still exists as one arrives at

different answers using different arguments, and a question still remains whether or not does an infinite ladder network converge to a pure resistance drawing continuous power from an input source, and if so where does this energy go. What could be the missing factor, if any, in these arguments?

5. Resolution of the paradox – incident versus reflected waves

Here we demonstrate with a detailed analysis that the resolution of the paradox lies in the realization that there is an absence of a reflected wave in an infinite ladder network or an infinite transmission line. Then we shall also understand why the two alternate approaches led to two conflicting conclusions.

5.1. The case of an infinite ladder network

5.1.1. The ladder network at low frequencies For frequencies below a critical value $\omega_0 = 2/\sqrt{LC}$, the characteristic impedance $Z_0 = \sqrt{L/C - \omega^2 L^2/4}$ can be written as $Z_0 = (\omega L/2)\sqrt{(\omega_0/\omega)^2 - 1}$, which is a *real* quantity, meaning a pure resistance. Let us consider the propagation factor $e^{-\gamma}$ between adjacent blocks calculated by terminating the ladder network in Z_0 . This is only to ensure that there is no reflected wave and thus one is dealing only with the incident wave. In the low frequency ($\omega < \omega_0$) case one gets [1, 4],

$$\frac{V'_n}{V'_{n-1}} = \frac{I'_n}{I'_{n-1}} = \frac{\sqrt{L/C - \omega^2 L^2/4} - j\omega L/2}{\sqrt{L/C - \omega^2 L^2/4} + j\omega L/2}. \quad (18)$$

We can simplify the Eq. (18) to get,

$$\frac{V'_n}{V'_{n-1}} = 1 - \omega^2 LC/2 - j\sqrt{\omega^2 LC}\sqrt{1 - \omega^2 LC/4} \quad (19)$$

$$= 1 - 2(\omega/\omega_0)^2 - j2(\omega/\omega_0)\sqrt{1 - (\omega/\omega_0)^2}. \quad (20)$$

A prime (') over voltages and currents merely indicates that these represent an incident wave. From the real and imaginary parts in Eq. (20), it can be readily seen that the propagation factor has a unit magnitude and represents a simple phase change $e^{-j\beta} = \cos \beta - j \sin \beta$, between successive blocks in the network.

Although for calculating the propagation factor of the circuit we needed to isolate the *incident wave* by terminating this network with its characteristic impedance Z_0 , yet the propagation properties of the incident wave (that is, the propagation constant calculated from Eq. (20) of *incident* wave between two neighboring blocks, say, $n-1$ and n) does not depend upon this termination. The incident wave has an input impedance everywhere equal to the characteristic impedance Z_0 of the network. Of course the voltages and currents at any point are decided by the superposition of the incident and reflected waves at that point and the input impedance of a network as calculated in [6, 9, 10, 11] is actually what results from the superposition of the incident and the reflected wave with their phases duly taken into account.

To prove our assertion that this indeed is the case in general, we want to calculate input impedance of an open-circuit line, made of any finite number of blocks (say, n), by evaluating voltage and current at $z = 0$ due to the sum of the incident and reflected waves, the latter arising from the termination just after the n th block. For a cascaded network of n identical blocks, the propagation factor is simply $e^{-jn\beta}$. The angle β here is half of θ defined in Eq. (21) of that in [9]. If the network has a total of n blocks, then voltage V_0 at $z = 0$ includes a reflected wave with a phase change of angle $2n\beta$ from the incident wave, while the current I_0 has a phase change of angle $2n\beta + \pi$ (an extra phase of angle π in the current wave at the reflection point). Therefore the input impedance is given by,

$$Z_i = V_0/I_0 = Z_0 \frac{1 + e^{-j2n\beta}}{1 - e^{-j2n\beta}} = -jZ_0 \cot(n\beta). \quad (21)$$

We see that the calculated input impedance is the same what was calculated in an alternative method for a finite open-circuit ladder network [9, 10], which thus proves our assertion that the propagation factor of the incident wave is unaffected by the termination impedance. As n is increased, Z_i is always of an *imaginary* value which goes through cycles, even becoming 0 or ∞ , and in general does not converge to a unique value even when $n \rightarrow \infty$.

5.1.2. Energy transport - a physical perspective In a finite open-circuit network there is a reflected wave from its terminated end as it has to match the conditions for a zero net current (implying the electric currents out of phase by angle π for the incident and the reflected waves), although the voltages will be in phase for the incident and reflected waves at the termination point. It is important to note that when we analyze a *finite* network, barring transients, the voltages and currents being considered are the superposition of incident and reflected waves. Therefore the calculated Z_i may depend upon the length of the line or equivalently the number of blocks in the network as that would determine the relative phases of the incident and reflected waves at the input point.

Suppose a generator is connected to the circuit at input terminals AA (Fig. 2(a)). The generator drives the circuit at a frequency ω (say) and will give rise to a voltage as well as a current in the 1st electric block, which (a pure reactance) does not consume the electric power itself, and in turn gives rise to voltage and current in the 2nd block and so on. As we showed above, for $\omega < \omega_0$, there will be no decrease in the amplitude of voltage or current from one block to the next and there will only be a progressive phase change from one block to the next. This “incident wave” will move along the network until a discontinuity, say an open-circuit termination after n th block, is encountered which will cause a reflection wave towards the block $n - 1$, then $n - 2$ and so on towards the generator.

The generator meanwhile will keep on supplying further power to the 1st block which gets passed forward, till it is finally reflects back towards the generator. This is true even when the line terminates just after block one (just a simple LC circuit, see

Appendix). And when we add more blocks, then the discussion still entails reflected waves implicitly. However when we consider an infinite ladder network or an infinite transmission line, all by itself (and not by an indefinite extension of finite network by adding more blocks or increasing length of the line), then we do not consider the reflected wave since the incident wave does not ever reach the termination point to start a reflected wave.

In that case we have only the incident wave and the source at the input keeps on continuously supplying power to the network or line but does not get it back through reflected wave. Therefore in an infinite network, it results in a net power drain from the source and this energy of course appears from one block to the next down the line where it has not yet reached due to the long extent of the line. Of course as it will never reach a termination point (at infinity!), so the energy transfer to further blocks continues for ever. Initially none of the blocks had electric energy (say just before time $t = 0$ when the generator was just connected), but afterwards up to a certain stage the blocks have stored electric energy (shared between its capacitor and inductor or equivalently between the electric and magnetic fields and getting continuously exchanged between them). Ultimately this energy has come from the generator. The energy is not lost as it can be still consumed by terminating the circuit in a matched load somewhere down the line or recovered by terminating the line as an open circuit and getting the energy returned as a reflected wave.

5.1.3. The ladder network at high frequencies The propagation factor $e^{-\gamma}$ between adjacent blocks, for a high frequency ($\omega > \omega_0$) case can be written as,

$$\frac{V'_n}{V'_{n-1}} = 1 - 2(\omega/\omega_0)^2 + 2(\omega/\omega_0)^2 \sqrt{1 - (\omega_0/\omega)^2}. \quad (22)$$

From Eq. (22) it can be seen that for $\omega > \omega_0$ the propagation factor, written as $e^{-(\alpha+j\pi)} = -(\cosh \alpha - \sinh \alpha)$, is of magnitude less than unity and is always of a negative value, implying a phase change of angle π between successive blocks accompanied by an exponential decrease in amplitude. The voltages and currents do not penetrate too far in the circuit, and there is no continuous transport of energy along z . The input impedance at frequencies $\omega > \omega_0$ for a cascade network of n blocks is,

$$Z_i = V_0/I_0 = Z_0 \frac{1 + e^{-2n\alpha}}{1 - e^{-2n\alpha}} = Z_0 \coth(n\alpha), \quad (23)$$

which is imaginary, in spite of $\coth(n\alpha)$ being always a real value. This is because the characteristic impedance $Z_0 = (j\omega L/2)\sqrt{1 - (\omega_0/\omega)^2}$ is imaginary for $\omega > \omega_0$. While the incident wave alone presents a *real* input impedance for frequencies $\omega < \omega_0 = 2/\sqrt{LC}$, when a superposition of incident and reflected waves is considered then we get an *imaginary* input impedance for all driving frequencies. That means the current at the input will be $\pi/2$ out of phase with the voltage, so that there will be no continuous power being absorbed from the source. For $n \rightarrow \infty$, $Z_i \rightarrow Z_0$, a pure reactance, thus there is no paradox for the $\omega > \omega_0$ case.

5.2. Infinite transmission line

The characteristic impedance of a ladder network in case of a lossless ideal transmission line with distributed parameters (Fig. 1) could be written as $Z_0 = \sqrt{(L\Delta z)/(C\Delta z) - \omega^2 L^2(\Delta z)^2/4}$ which reduces to $Z_0 = \sqrt{L/C}$ as in limit $\Delta z \rightarrow 0$. Therefore unlike the ladder network case, in the transmission line case there is no cutoff frequency and for *all* driving frequencies a wave travels along the line without any amplitude attenuation since propagation constant has an *imaginary* value implying only a phase change.

In general the input impedance of a line of length l is given by [1],

$$Z_i = Z_0 \left(\frac{e^{\gamma l} + K e^{-\gamma l}}{e^{\gamma l} - K e^{-\gamma l}} \right), \quad (24)$$

where K (=reflected voltage at load/incident voltage at load) is the reflection coefficient,

$$K = \left(\frac{Z_r - Z_0}{Z_r + Z_0} \right). \quad (25)$$

where Z_r is the impedance at the receiving (load) end. The input impedance reduces to Z_0 when there is no reflected wave, i.e., when $K = 0$.

Now the absence of a reflected wave in a transmission line can be due to three reasons. First, the line is finite but terminates in a load matched to the characteristic impedance of the line, i.e., when $Z_r = Z_0$. Second, the line has small resistance which can causes the incident voltage to die over its long length l , i.e., if $\gamma l \rightarrow \infty$, so that the amplitude of the incident and thence of the reflected wave is zero, then the series does converge to a unique solution [6, 11] which is consistent with $Z_i = Z_0$. Thirdly the line is lossless but truly of infinite extent so that it could be assumed that the incident wave, which assumedly started a finite time back, has not yet reached the termination point to start a reflected wave. In all three cases, the input impedance, which is the ratio of the voltage and current at the input point, is the same as that is not affected by what happens at its termination point, and we obtain the same result for the input impedance, viz. $Z_i = Z_0$.

On the other hand, for an open-circuit line of finite length l ($Z_r = \infty$, $K = 1$), the input impedance is given by,

$$Z_i = Z_0 \left(\frac{e^{\gamma l} + e^{-\gamma l}}{e^{\gamma l} - e^{-\gamma l}} \right). \quad (26)$$

In a lossless line, $\gamma = j\beta = j\omega\sqrt{LC}$, the input impedance becomes,

$$Z_i = Z_0 \left(\frac{e^{j\beta l} + e^{-j\beta l}}{e^{j\beta l} - e^{-j\beta l}} \right) \quad (27)$$

$$= -jZ_0 \cot(\beta l) = -jZ_0 \cot(2\pi l/\lambda), \quad (28)$$

which is a pure reactance, and thereby no net power consumed, and which is similar to the result derived for the ladder network Eq. (21). It should be noted that in case of a ladder network, the quantities γ, α, β , or even L, C etc. are specified as per block of the circuit while in the case of a transmission line with distributed parameters all such

quantities are defined per unit length of the line. Therefore in Eq. (21) it is the phase angle change $n\beta$ over n blocks while in Eq. (28) it is the phase angle change βl over length l of the line. In fact with increasing l , Z_i/Z_0 from Eq. (28) is cyclic and is indeed the value read from the Smith chart. One thing that we notice from Eq. (28) is that the input impedance Z_i depends on the length l of the line in terms of wavelength λ . Thus depending upon $2\pi l/\lambda$, Z_i could be zero, a finite value or even infinity, but always a pure *imaginary* value, with a zero *real* part similar to what was seen for the ladder network in IV.A.1. Here as much amount of power is reflected back to the generator as much it supplies in the incident wave.

In the case where there is only an incident wave, i.e., there is no reflected wave, the current is in fact in phase with the voltage, implying power is being drawn from the source. However, if there is a reflected wave as well, then the voltage and current are not in phase everywhere. Thus it is the absence of reflected wave in infinite transmission line that results in a continuous positive energy flux along the line. The relative phases of V and I depend upon the reflected wave, which in turn depends upon at how far away along the line reflection took place. Of course no reflection will ever take place in a uniform infinite line as the incident wave will never reach the termination point which is at infinity. However if we consider the lossless case when there is a reflected wave from an open-circuit termination, then equal power is being returned to the source by the reflected wave and in that case the current is indeed $\pi/2$ out of phase with the voltage (Eqs. (21) and (28)).

If we consider a transmission line with no discontinuities whatsoever, then it will have to be an infinite line and the energy will be getting stored as electric and magnetic fields in its reactive elements further and further along the line. There is no violation of the energy conservation, and since there is no reflected wave to restore energy to the source, the latter would be continuously supplying energy, which gets stored in electric and magnetic fields in more and more inductances and capacitances down the line. Seen this way there does not seem to be any paradox.

The paradox actually had arisen only because we were comparing two sets of solutions which are for quite different situations. One involves only an incident wave (i.e., without any reflected wave) and then the input impedance $Z_i = Z_0$ is a *real* quantity, and the voltages and currents are in phase everywhere along the circuit, with energy getting apparently “spent” as it is getting stored in the inductors and capacitors down the line as the incident keeps on advancing for ever in an infinite transmission line. The other solution was for the case with a reflected wave, and there the superposition of the incident and reflected waves results in Z_i to have *imaginary* value with no *net* power loss since the source gets the energy back as the reflected wave.

6. Conclusions

It was shown that while an open-circuit finite ladder network or a transmission line with distributed network has a characteristic impedance z_0 which is only reactive (imaginary),

an infinite ladder network or an infinite transmission line has a finite *real* component of the input impedance. It was shown that the famous paradox of power loss in a lossless infinite transmission line is successfully resolved when one takes into account both the incident and reflected waves. The solution of the paradox lies in the realization that there is an absence of a reflected wave in an infinite transmission line. In a finite transmission line or ladder network, the source still keeps on supplying power as an incident wave but gets it equally back in terms of the reflected wave. Therefore there is no further net power transfer from the source which is consistent with the reactive elements presenting zero net resistance.

However in the case of an infinite ladder network or an infinite transmission line there is no discontinuity to start a reflected wave, thus the source supplies power in a forward direction, but does not get it back in terms of a reflected wave from the termination point. Therefore there is an apparent net power loss, which actually appears as stored energy in its reactive elements (capacitances and inductances) further down the line. It was also shown that radiation plays absolutely no role in resolving this paradox.

7. Appendix

Input impedance of a driven LC circuit computed from a superposition of incident and reflected waves

Here we explicitly demonstrate that a driven LC circuit can be treated as an open-circuit 1-block ladder network having incident and reflected waves and from their superposition, the voltages and currents, and in particular, input impedance of the LC circuit can be calculated for all driving frequencies. We denote by V_0, I_0 and V_1, I_1 the voltages and currents at the input (AA) and termination (BB) respectively, and which (Fig. 3(a)) are related by $V_0 - V_1 = j\omega LI_0/2$, $I_0 = j\omega CV_1$, where ω is the frequency at which the circuit is being driven by, say, a generator at the input end AA. The input impedance $Z_i = V_0/I_0$ is given by,

$$Z_i = j\omega L/2 + 1/(j\omega C). \quad (29)$$

Denoting voltages and currents for the incident and reflected waves by V', I' and V'', I'' respectively, the boundary conditions at open end BB in Fig. (3a) imply $V_1'' = V_1'$ and $I_1'' = -I_1'$, the minus sign arising because the reflected current is out of phase with the incident wave by an angle π , so as to make the net current $I_1 = I_1' + I_1'' = 0$. However to evaluate I_1' , we need to isolate the incident wave and which can be done by terminating the circuit in its characteristic impedance Z_0 (Fig. 3(b)). The propagation factor for the incident wave from Eq. (19) is,

$$\frac{V_1'}{V_0'} = \frac{I_1'}{I_0'} = 1 - \omega^2 LC/2 - j\sqrt{\omega^2 LC} \sqrt{1 - \omega^2 LC/4}, \quad (30)$$

with $V_0'/I_0' = V_1'/I_1' = Z_0$. As demonstrated in IV.A.1, incident wave is not attenuated, irrespective of the termination impedance. The only difference is that there is also a

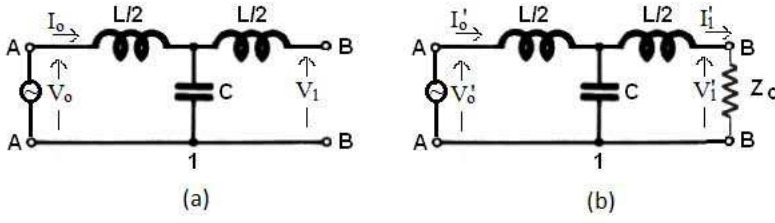


Figure 3. A driven LC Circuit or a single-block network (a) open-circuited (b) terminated in its characteristic impedance Z_0 and thereby carrying only the incident voltage and current with no reflection at the end BB.

reflected wave in the open circuit case (Fig. 3(a)), while there is no reflected wave when the circuit is terminated in its characteristic impedance Z_0 (Fig. 3(b)).

For the reflected wave in Fig. 3(a) one can write the propagation factor as,

$$\frac{V_0''}{V_1''} = \frac{I_0''}{I_1''} = 1 - \omega^2 LC/2 - j\sqrt{\omega^2 LC} \sqrt{1 - \omega^2 LC/4}. \quad (31)$$

Equation (30) can be rewritten as,

$$\frac{V_0'}{V_1'} = \frac{I_0'}{I_1'} = 1 - \omega^2 LC/2 + j\sqrt{\omega^2 LC} \sqrt{1 - \omega^2 LC/4}, \quad (32)$$

From Eqs. (31) and (32) we get for the voltage V_0 and current I_0 as the superposition of the incident and reflected waves,

$$V_0 = V_0' + V_0'' = 2V_1'(1 - \omega^2 LC/2) \quad (33)$$

$$I_0 = I_0' + I_0'' = 2I_1' j\sqrt{\omega^2 LC} \sqrt{1 - \omega^2 LC/4} \quad (34)$$

Therefore we get the input impedance Z_i as,

$$Z_i = V_0/I_0 = \frac{V_1'}{I_1'} \frac{1 - \omega^2 LC/2}{j\sqrt{\omega^2 LC} \sqrt{1 - \omega^2 LC/4}} \quad (35)$$

Using $Z_0 = \sqrt{L/C - \omega^2 L^2/4} = \sqrt{L/C} \sqrt{1 - \omega^2 LC/4}$, we get $Z_i = j\omega L/2 + 1/(j\omega C)$, which of course is the expected result Eq. (29). The input impedance is *imaginary* for all driving frequencies.

Acknowledgements

I thank Prof. S. C. Dutta Roy of IIT Delhi for his comments and suggestions on the manuscript.

References

- [1] Ryder J D 1955 *Network, Lines and Fields* 2nd edn (Englewood Cliffs, NJ: Prentice Hall) chapter 6
- [2] Jordan E D and Balmain K G 1968 *Electromagnetic Waves and Radiating Systems* 2nd edn (Englewood Cliffs, NJ: Prentice Hall) chapter 7

- [3] Ramo S Whinnery J R and Duzer T V 1965 *Fields and Waves in Communication Electronics* (New York: Wiley) chapter 1
- [4] Feynman R P 1964 *Lectures on Physics* Vol 2 (Reading, MA: Addison-Wesley) chapter 22
- [5] Dutta Roy S C 2007 Paradoxical behaviour of an infinitely long loss-less transmission Line *Proc. Indian Natn. Sci. Acad.* **73** 33-36
- [6] van Enk S J 2000 Paradoxical behavior of an infinite ladder network of inductors and capacitors *Am. J. Phys.* **68** 854-856
- [7] Dykhne A M Snarskiĭ A A and Zhenirovskii M I 2004 Stability and chaos in randomly inhomogeneous two-dimensional media and LC circuits *Physics - Uspekhi* **47** 821-828
- [8] Keskin A U Pazarci D and Acar C 2005 Comment on ‘Paradoxical behavior of an infinite ladder network of inductors and capacitors’ by S J van Enk [2000 *Am. J. Phys.* *68* 854-856] *Am. J. Phys.* **73** 881-88
- [9] Ucak C and Acar C 2007 Convergence and periodic solutions for the input impedance of a standard ladder network *Eur. J. Phys.* **28** 321-329
- [10] Ucak C and Yegin K 2008 Understanding the behaviour of infinite ladder networks *Eur. J. Phys.* **29** 1201-1209
- [11] Krivine H and Lesne A 2003 Phase transition-like behaviour in a low-pass filter *Am. J. Phys.* **71** 31-33
- [12] Ramm A G and Weaver L 2004 Explanation of Feynman’s paradox concerning low-pass filters *Int. J. Appl. Math. Sci.* **1** 111-116